

Carr Head Primary School - Knowledge Organiser

Science

Electricity

Year 6

Summer 1

Key Knowledge

Circuit Electricity can flow through components in a complete electrical circuit. A circuit needs a power source, such as a battery, with wires connected to both the positive (+) and negative (-) ends. A battery is made from a collection of cells connected together. A circuit can also contain other electrical components, such as bulbs, buzzers or motors, which allow electricity to pass through.

Electrical components A component is a part of an electrical circuit.

Circuit diagram When drawing circuit diagrams, rather than drawing detailed components, we use simple symbols to represent the different components.

Current Current is the flow of an electric charge. It flows through a circuit when a voltage is placed across two points of a conductor.

Low resistant route Electricity follows the path of least resistance. Some materials have low resistance and are conductors.

Electromagnet Electromagnets are created using electricity and a magnetic material such as iron, an iron nail is perfect for this example. When electricity passes through a copper wire it creates a magnetic field around the wire. By winding a coil of wire around an iron core you can increase the strength of the magnetic field produced and create an electromagnet.

Key Vocabulary

Electricity Electricity is an energy. It can be used to power electrical items such as toasters, kettles, T.V.s, etc. Electrical energy is caused by electrons (the

Symbols Circuits are drawn using symbols instead of drawing of the real equipment. This is to make the drawings easier. There are special symbols for everything that may be required in a circuit.

Fault An abnormal flow of electrical cur-

Series circuit A series circuit only has one path fir

Conductor Some materials are insulators, as

Magnetic field The magnetic field is the area around a magnet in which there is a mag-



Battery



Wire




Bulb



Buzzer



Motor

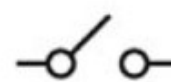

Switch (off)



Switch (on)

Know how to...

Working Scientifically

Systematically identifying the effect of changing one component at a time in a circuit.

Designing and making a useful circuit.

Planning different types of scientific enquiries to answer questions, including recognising and controlling variables where necessary.

Thomas Alva Edison (1847 – 1931) was an American inventor, most famous for inventing the long-lasting, practical lightbulb.

